

Exercício 05

1 - Alternativa A

2 – Alternativa **C)** **A=0, B=0, C=1**

3 – a)

$X = A \cdot B + \overline{C}$			
Tabela verdade			
A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

3 – b)

$$X = A \cdot B$$

Tabela verdade

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

3 – c)

$$Q = \overline{A \cdot B} + C$$

Tabela verdade

A	B	C	Q
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

4 – Alternativa C